



Justin Hsu

EEC 100 Lab 5

10/21/24

(1) Objective: Learn how to calculate, build, and simulate low pass, high pass, and band pass filter circuits. Then using the function generator see how different input frequencies are manipulated by each kind of filter. Finally using the data to create a bode plot to easily interpret at what frequencies the filters are attenuating the input.

(2) Prelab:

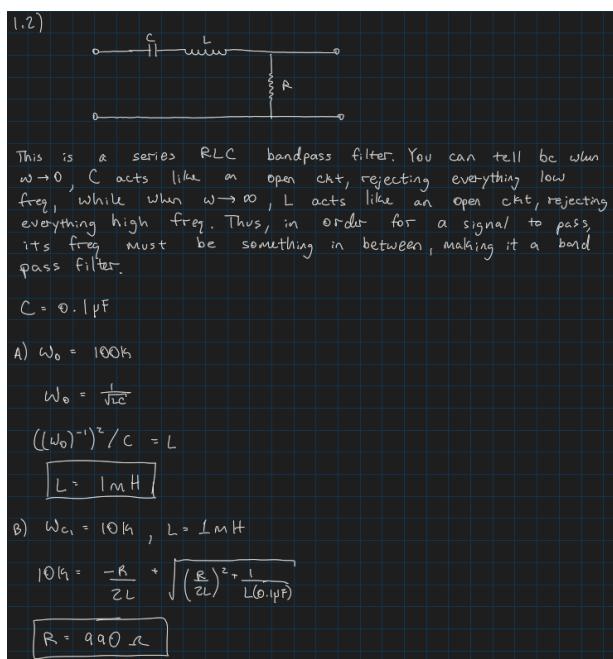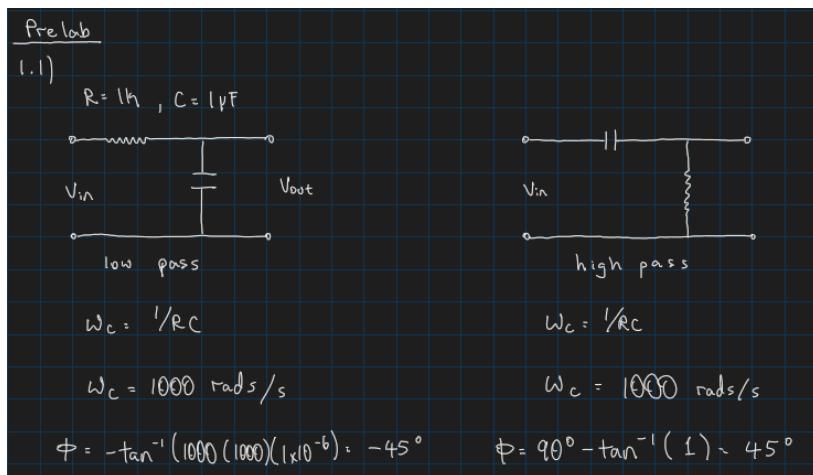


$$c) \omega_{c2} = 1 \text{ rad/s}$$

$$1 \text{ rad/s} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{L(0.1\mu F)}}$$

$$\boxed{R = 990 \Omega}$$
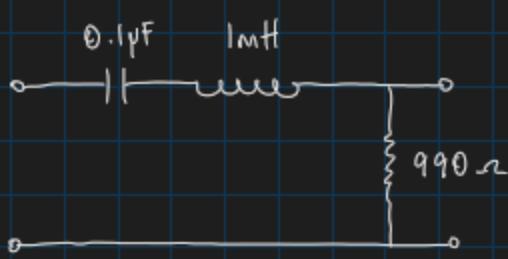
$$\phi = -\tan^{-1} \left( \frac{\omega L - \omega C}{R} \right)$$




$$\omega = 10 \text{ kHz}, \phi = 45^\circ$$

$$\omega = 100 \text{ kHz}, \phi = 0^\circ$$


$$\omega = 1 \text{ MHz}, \phi = -45^\circ$$

(3) Simulation:

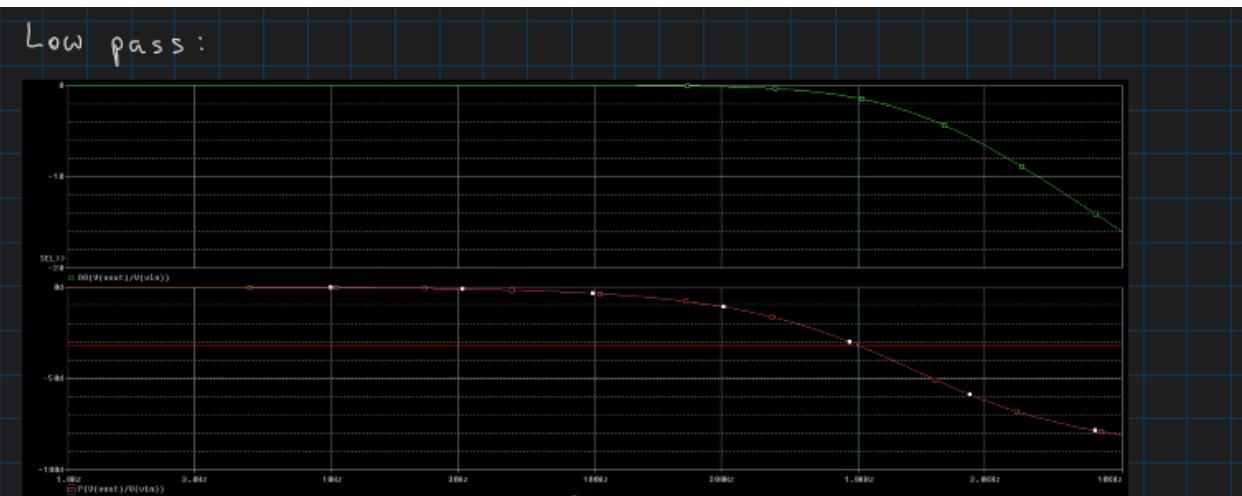


This agrees with my calculated  $\omega_c$  value, since in the magnitude plot we can see the magnitude start attenuating after 1 kHz.

High pass:

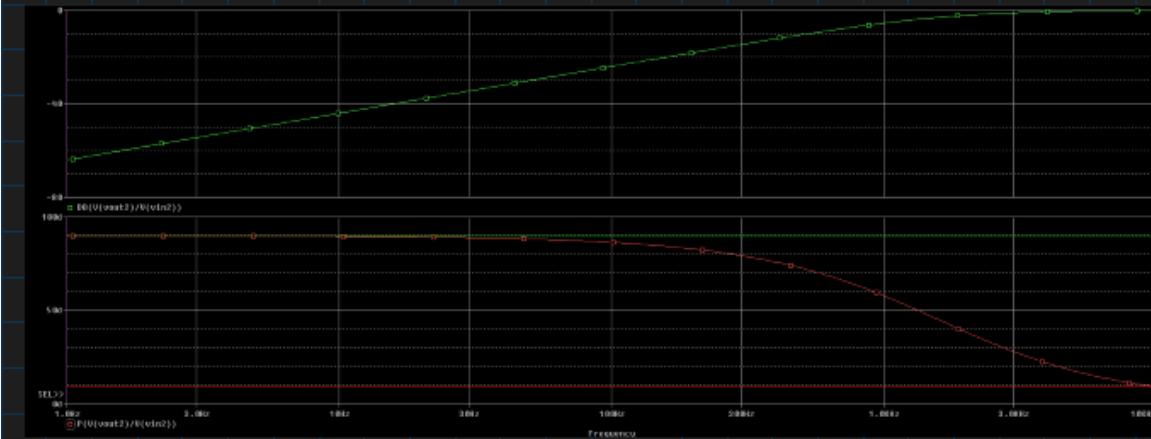

The magnitude plot agrees with my calculations as we can clearly see before 10kHz there is attenuation of the signal.



Bandpass:


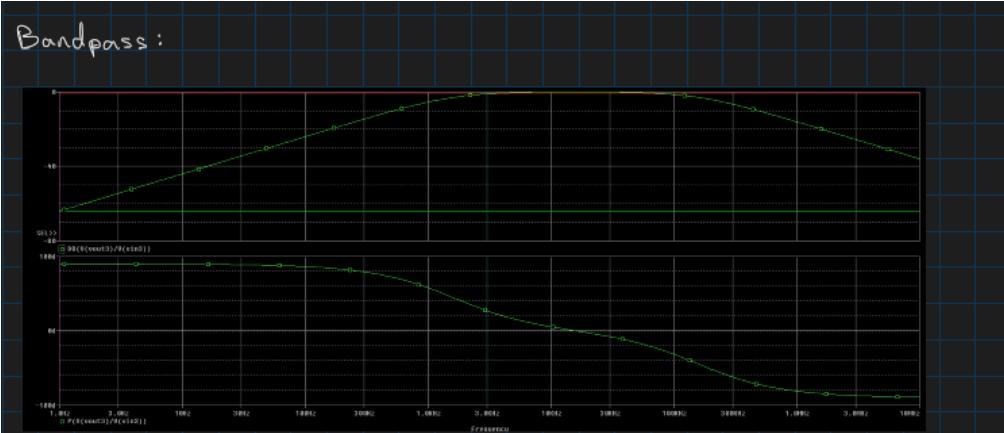




The magnitude plot agrees with my calculations as we can see that the signal with freq below 1.6kHz (10k rad/s) and above 160kHz (160k rad/s) is being attenuated. Furthermore, you can see that  $\omega_r$  is  $\sim 16$  kHz since that is where the max magnitude is.


The phase shift does make sense as @ 1.6 kHz (10k rad/s) there is a shift down to  $45^\circ$ , and @ 16 kHz (160k rad/s) is another shift down to  $0^\circ$ , and finally @ 160 kHz (1M rad/s) there is the final phase shift down to  $-45^\circ$ , which agrees with my calculations.


(4) Experiment:

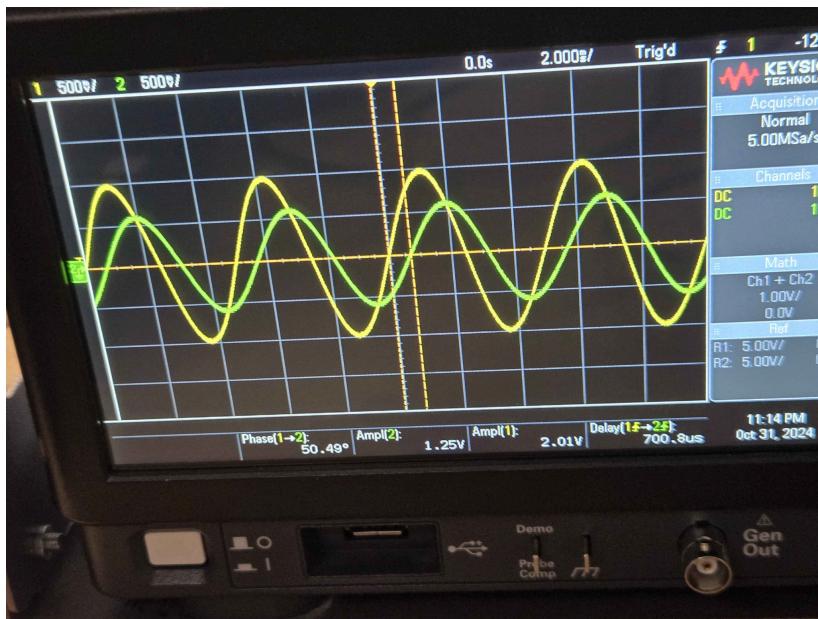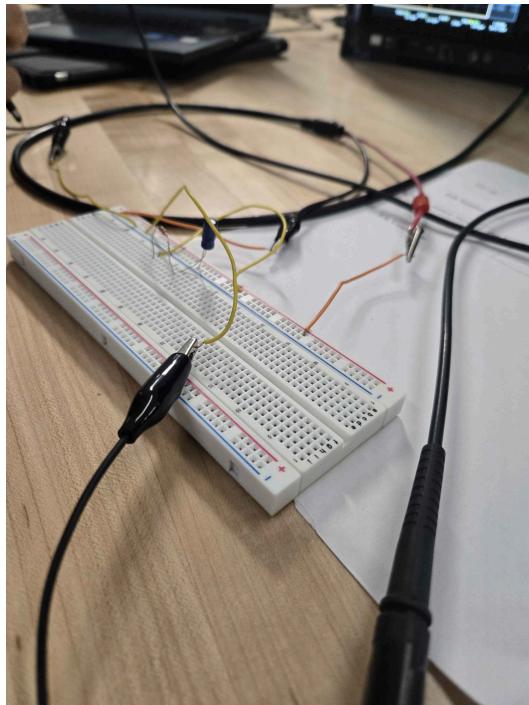

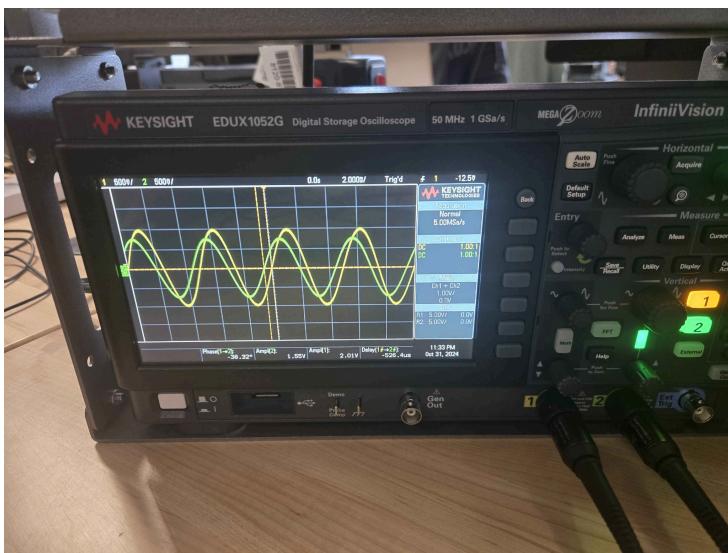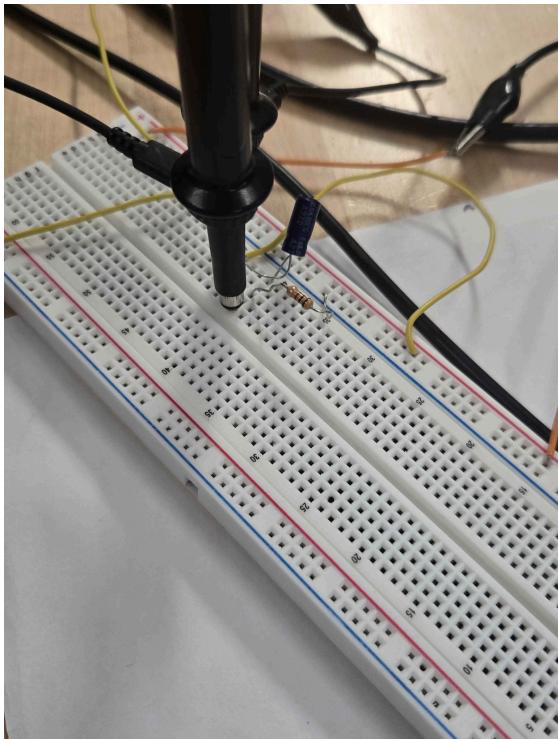

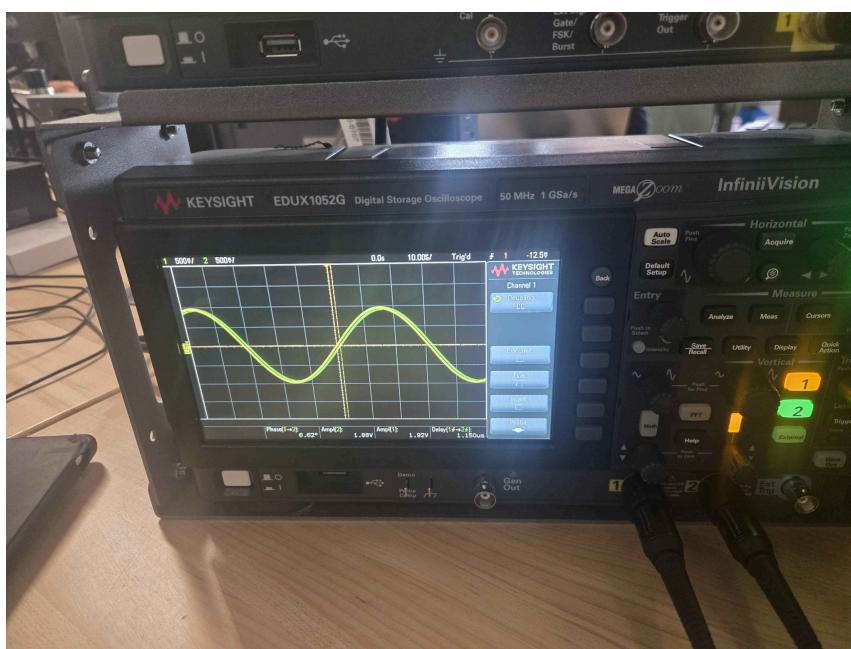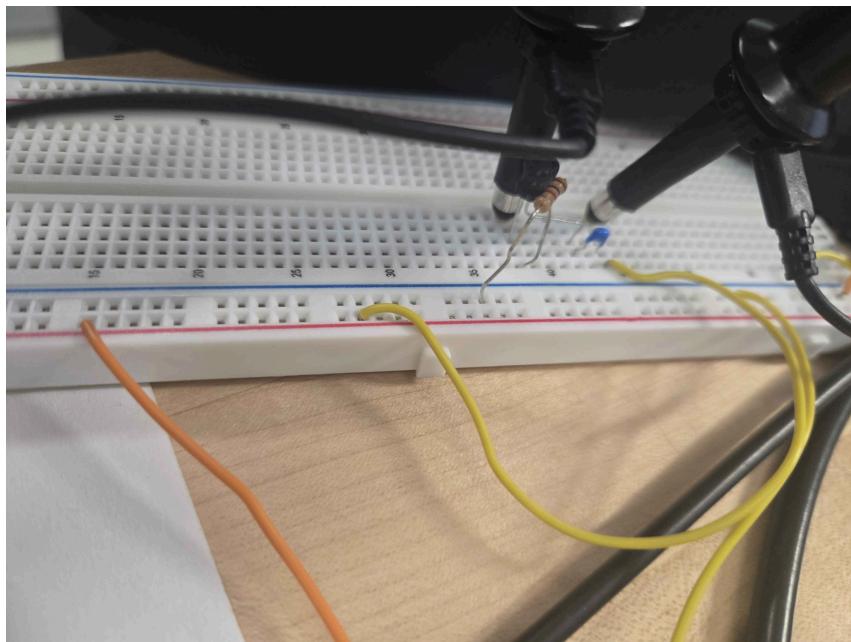

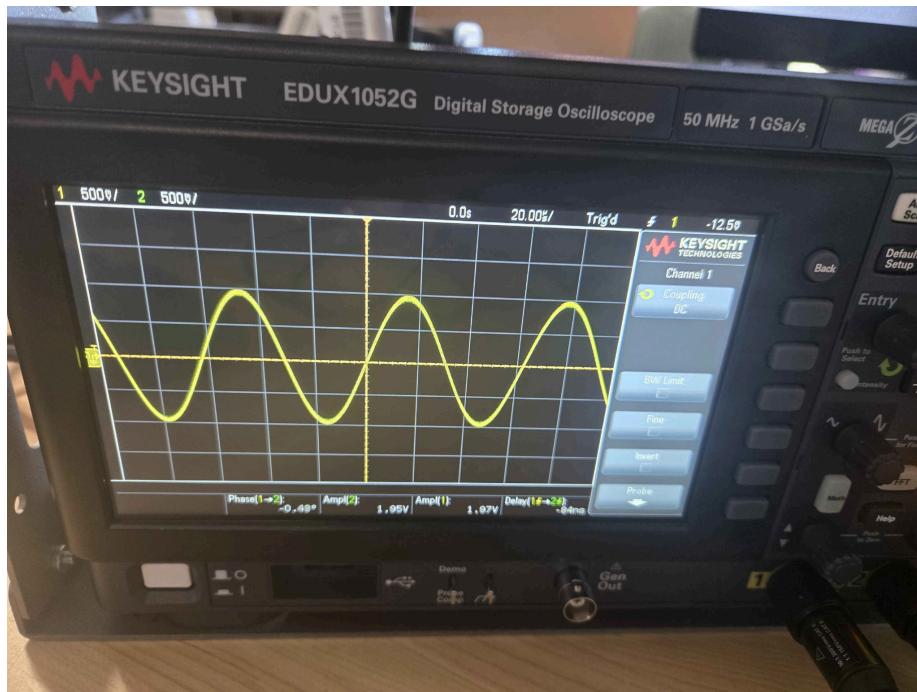

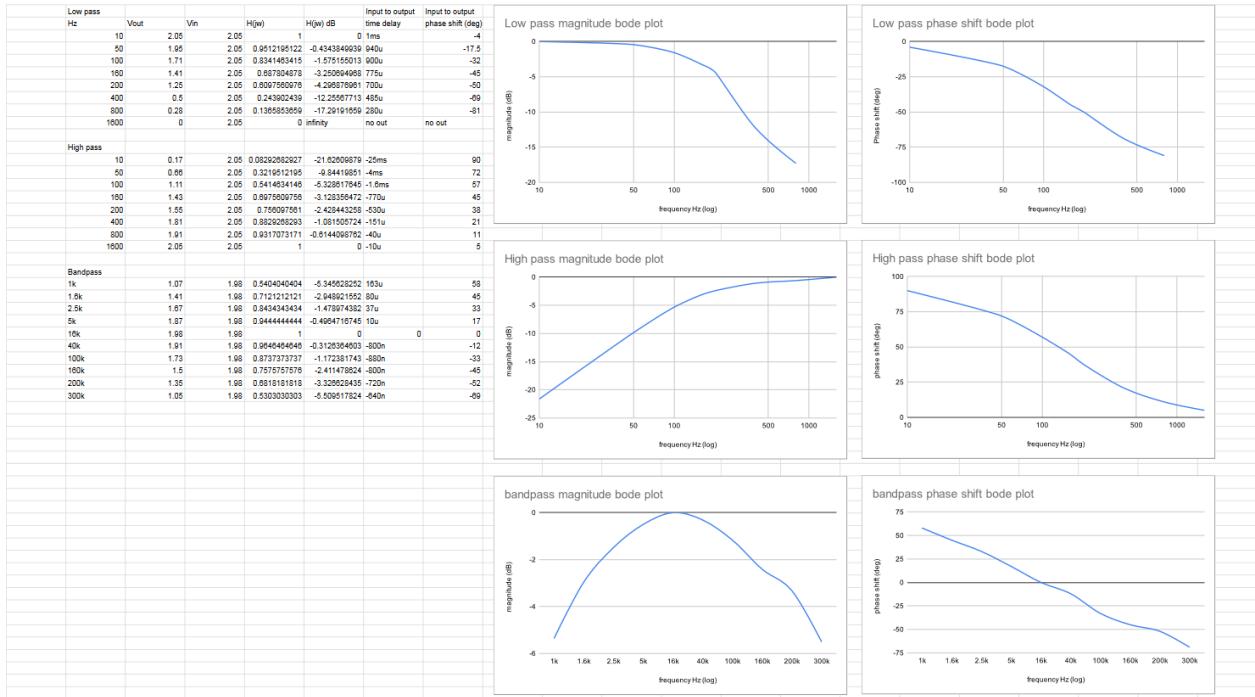

[Link to spreadsheet](#)

The experimental cut off values in the low pass filter matched our calculated results. It deviated slightly due to the inherent variance in resistor and capacitor values. Furthermore, the graphed bode plot from our experimental values matched the general shape of the simulated bode plot (there is a deviation because the x axis scaling did not match and there are not enough data points to create a smooth curve).

The experimental cut off values in the high pass filter matched our calculated results. It deviated slightly due to the inherent variance in resistor and capacitor values. Furthermore, the graphed bode plot from our experimental values matched the general shape of the simulated bode plot (there is a deviation because the x axis scaling did not match and there are not enough data points to create a smooth curve).

The experimental cut off values in the band pass filter matched our calculated results. It deviated slightly due to the inherent variance in resistor and capacitor values. Furthermore, the graphed bode plot from our experimental values matched the general shape of the simulated bode plot (there is a deviation because the x axis scaling did not match and there are not enough data points to create a smooth curve).

## (5) Conclusion:

Our calculated values and simulated values matched the experimental values found in lab. While there is deviation due to the deviation in resistance and capacitance values, the general shape of the bode plots matched, and the cut off values were within an acceptable margin of error. By inputting a signal of various frequencies into the filter circuits, we were able to see just how the various frequencies were manipulated by the filter-whether they were let through or attenuated. Through this experiment my understanding of how filter circuits work improved, and I can intuitively predict how a certain input signal will be affected by the filter circuit.

(6) Checkoff:

UNIVERSITY OF CALIFORNIA, DAVIS  
Department of Electrical and Computer Engineering

EEC 100

Circuits II

Fall 2024

Lab Number .....

Student Name	Pre-Lab	Simulation	Experiment	Total	T.A. Signature	Date
Daniel Narvich	B	B	B			16/31
Justam Hsu	B	B	B			16/31

T.A. Comments: