


Justin Hsu


EEC 100 Lab 8

11/27/24

(1) Objective: Learn how to use laplace transforms to deal with constantly changing circuit elements such as an inductor and capacitor without having to solve differential equations.

(2) Prelab:

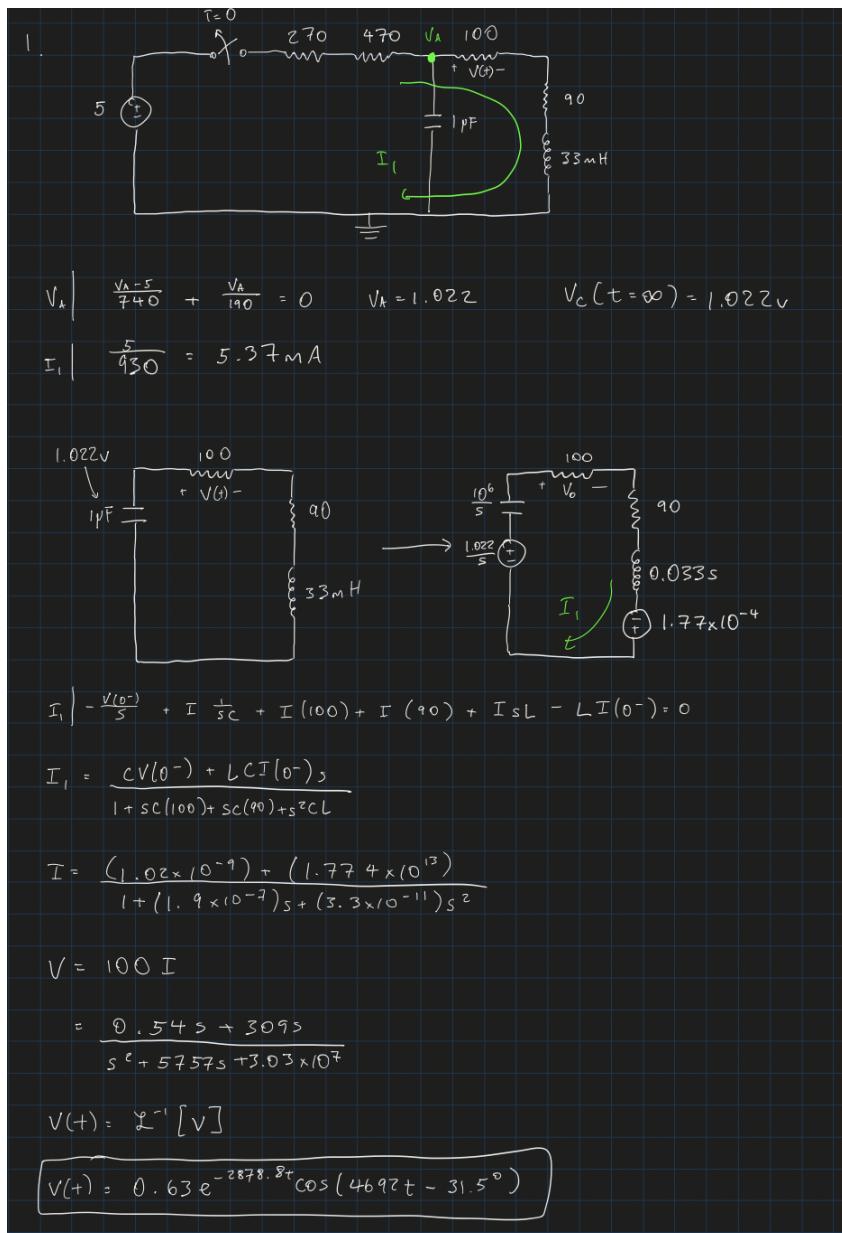

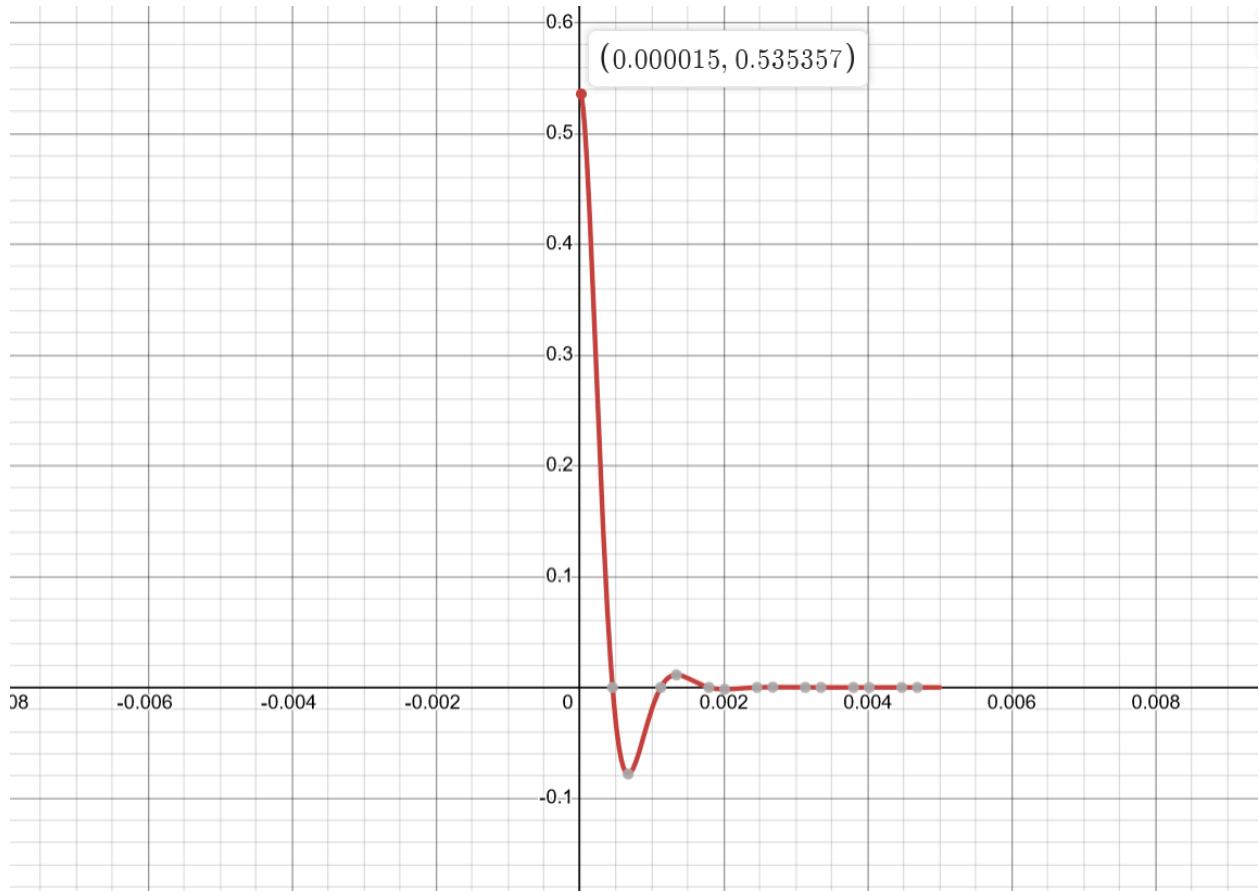

3.


$$V(t) = 0.535 \text{ J}$$

$$V(t=\infty) = 0 \text{ J}$$


$$V(t)_{\min} = -0.12 \text{ J}$$


$$T = 0.00067 \text{ to reach min}$$


### (3) Simulation:

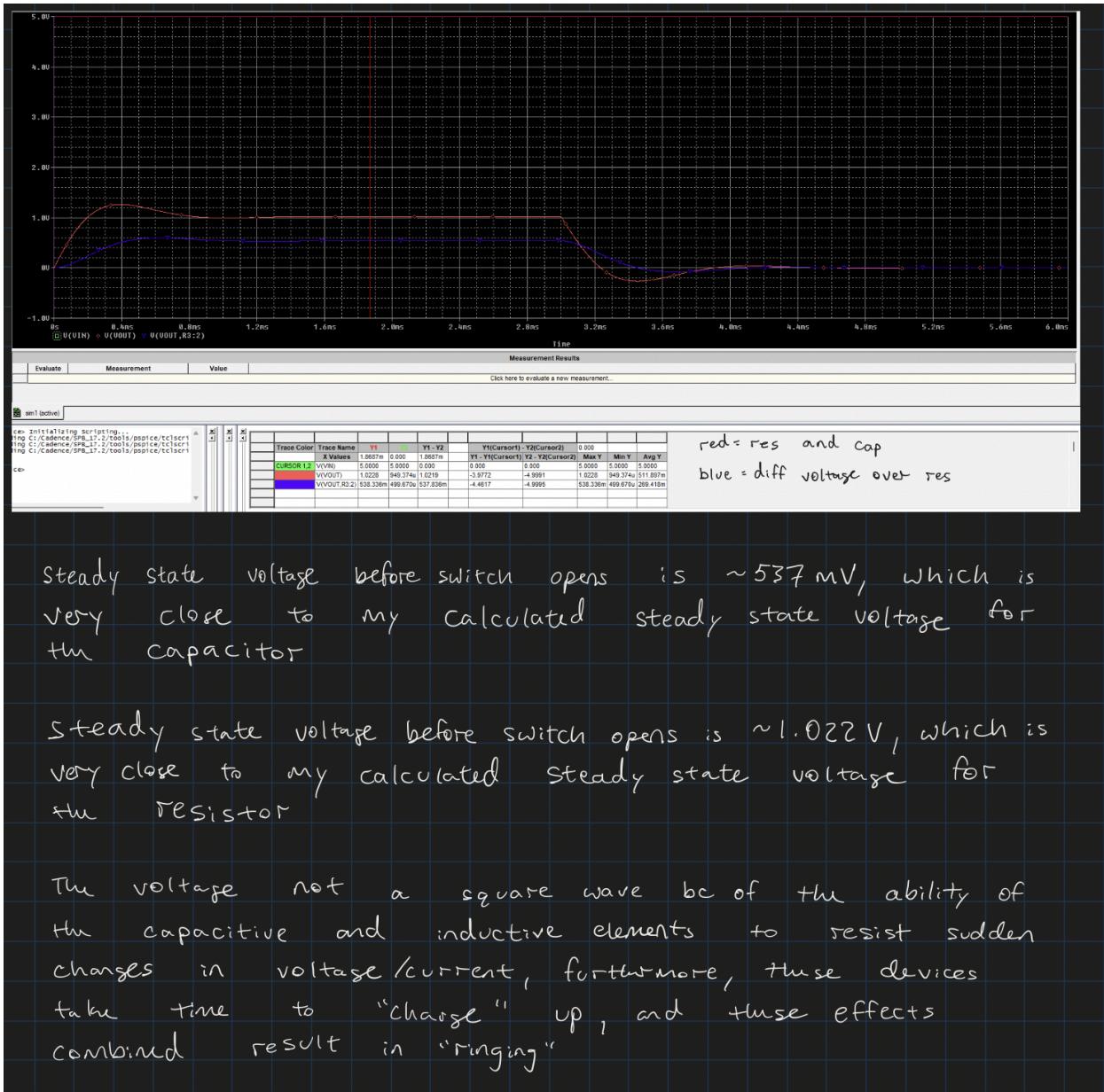



### (4) Experiment:

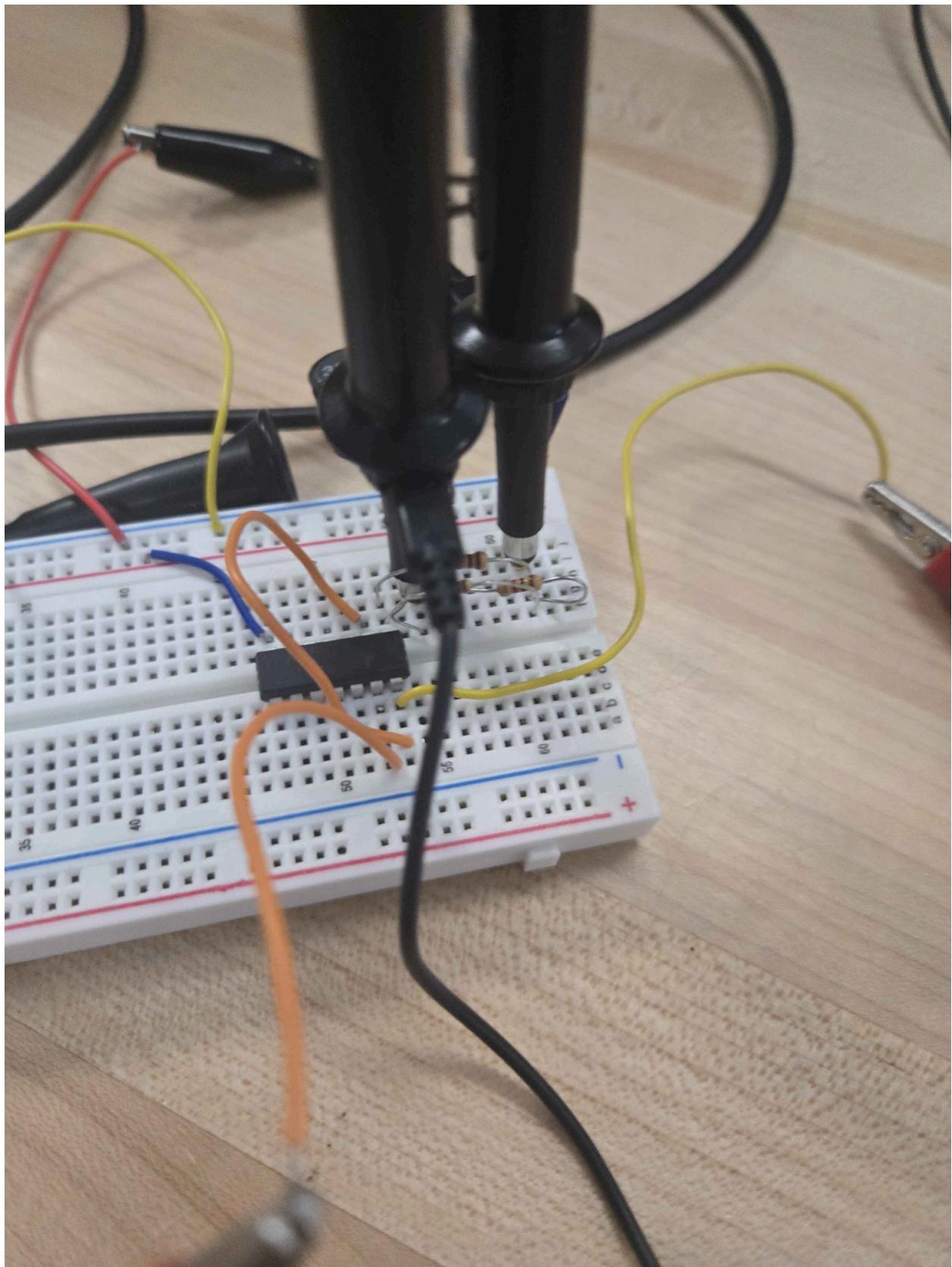

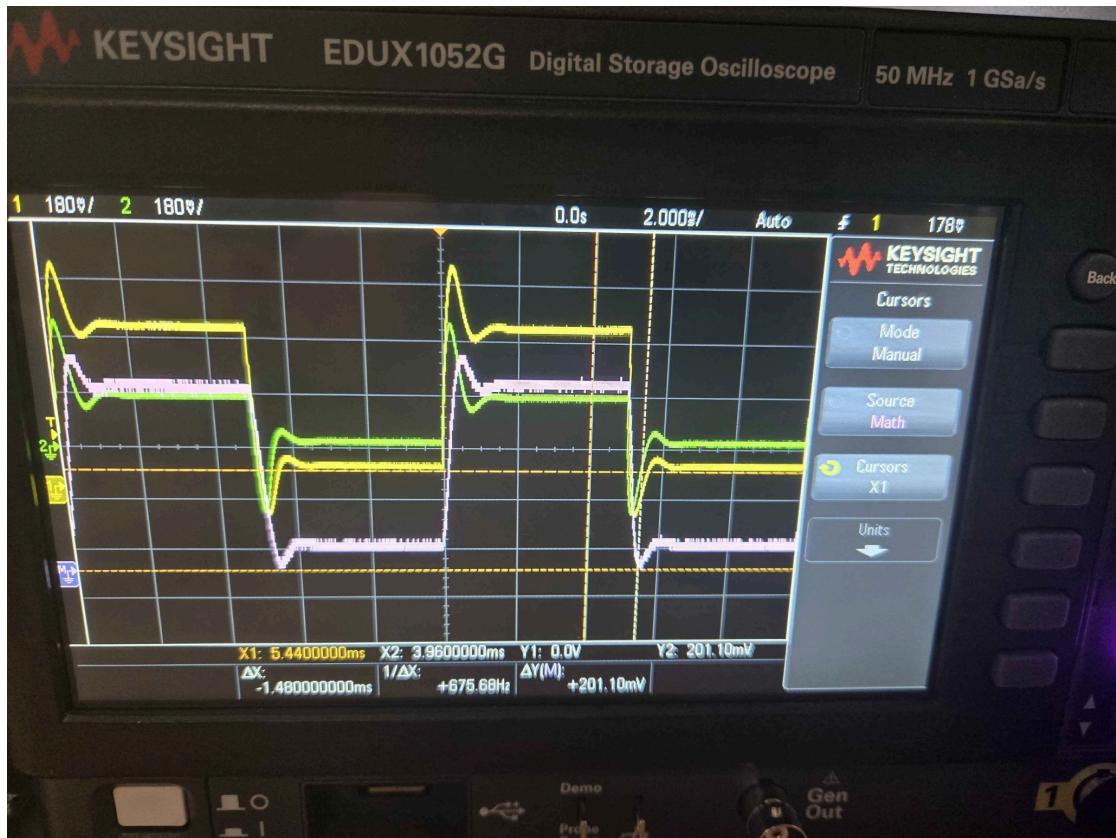

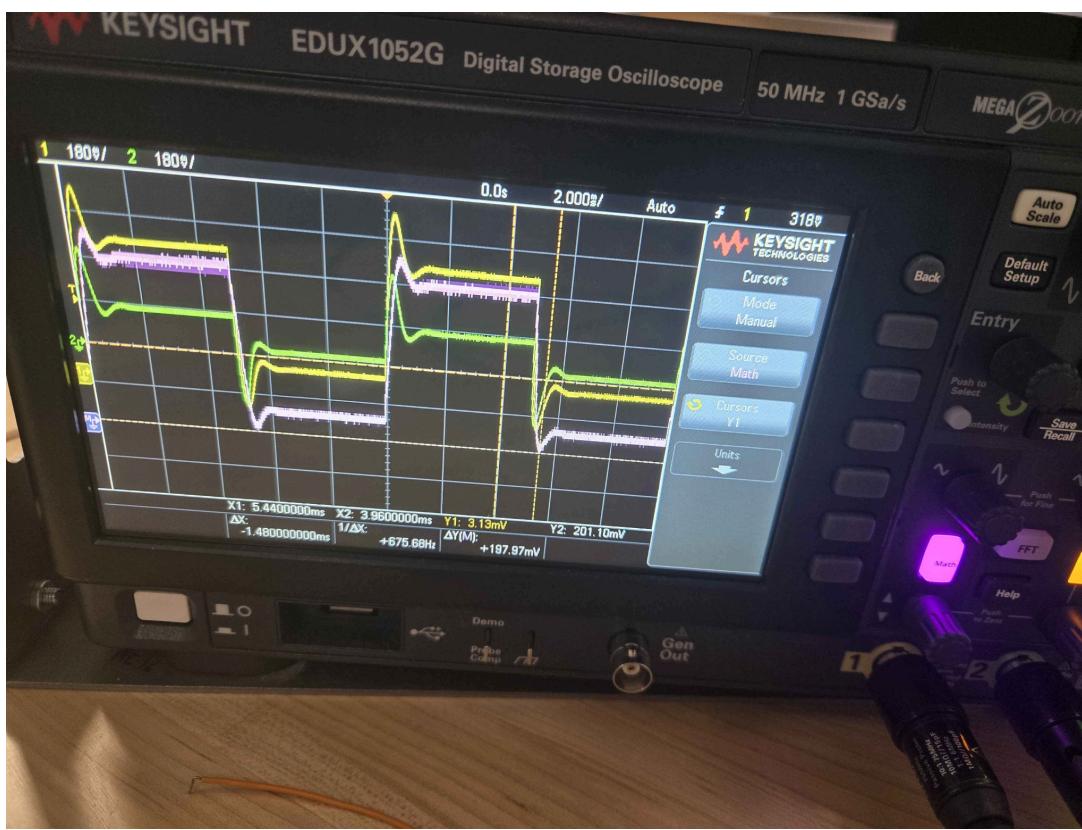

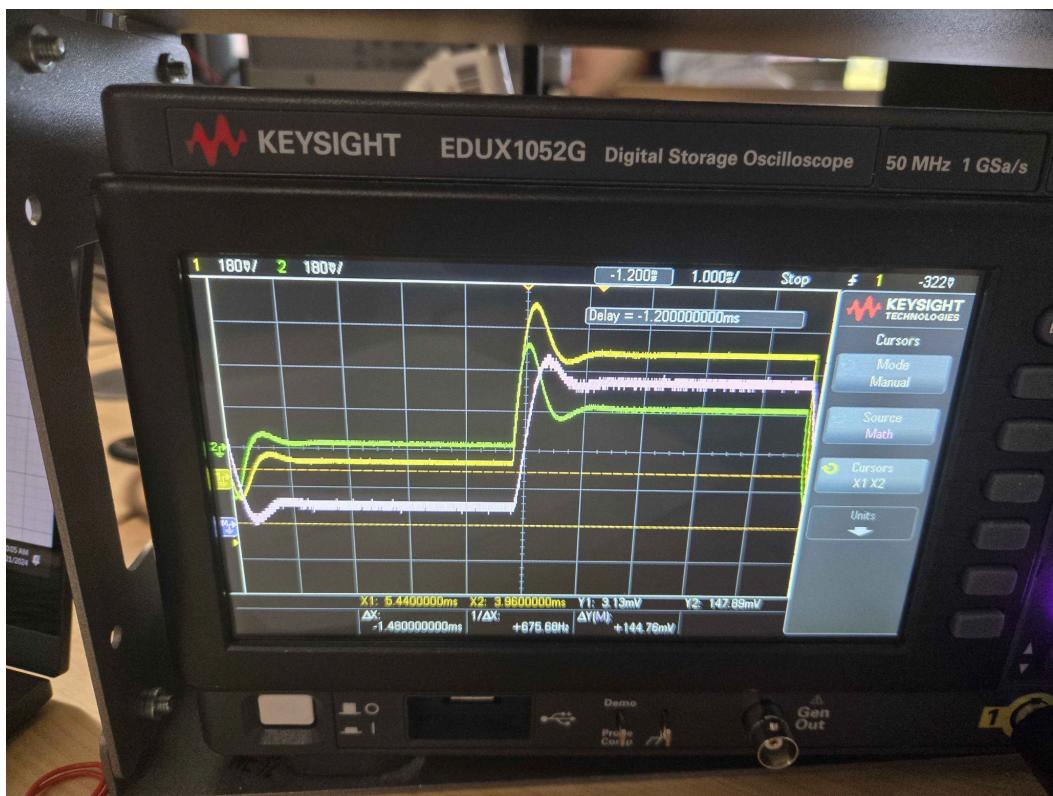

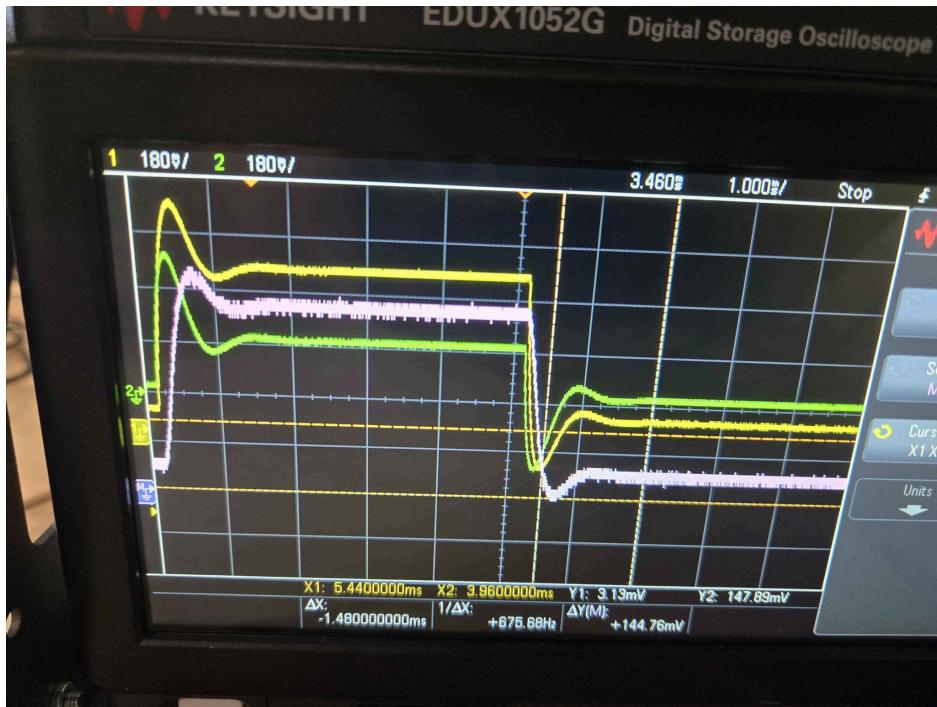

## (5) Conclusion:

Through using laplace transforms, I was able to calculate the voltage across a resistor in a RC circuit without having to solve difficult differential equations. My calculations were proven in lab by measuring the voltage across the resistor. However, due to not having 470 ohm resistors available, we had to use two 1000 ohm resistors in parallel to try and rectify it, and along with having other non idealities in the circuit such as varied capacitance and inductance values, and non ideal switch, our measurements were slightly off from the ideal results calculated from the prelab.

(6) Checkoff:

UNIVERSITY OF CALIFORNIA, DAVIS  
Department of Electrical and Computer Engineering

EEC 100

Circuits II

Fall 2024

Lab Number 8.....

Student Name	Pre-Lab	Simulation	Experiment	Total	T.A. Signature	Date
Daniel Narovich	R	R	R			11/21/24
Justin Hsu	R	R	R			11/21/24

T.A. Comments: