

Justin Hsu

EEC 100 Lab 6

11/13/24

(1) Objective: Learn how to calculate, build, and simulate an active bandpass filter. Then using the function generator see how the signal is attenuated or passed at certain frequencies. Finally creating a bode plot to easily interpret at what frequencies are the signals being attenuated.

(2) Prelab:

Prelab
1) active bandpass filter

$f_{c1} = 200 \text{ Hz} = 400\pi \text{ rad/s}$
 $f_{c2} = 20 \text{ kHz} = 40\text{k}\pi \text{ rad/s}$

Low pass cap = 2.4 nF
High pass cap = 800 nF

gain = $20 \text{ dB} \rightarrow 20 \text{ dB} : 20 \log(x) \quad x = e \rightarrow \text{gain} = \frac{R_{fo}}{R_{in}} = 10$

low pass high pass gain stage

$\omega_{c2} = \frac{1}{R_L C_L}$ $\omega_{c1} = \frac{1}{R_H C_H}$ $\omega_0 = \sqrt{\omega_{c1} \omega_{c2}}$

$400\pi = \frac{1}{R_H C_H}$ $C_H = 800 \text{ nF} \quad R_H = 994.72 \Omega$
 $40\text{k}\pi = \frac{1}{R_L C_L}$ $C_L = 2.4 \text{ nF} \quad R_L = 3315.73 \Omega$

$\omega_0 = 12566.37 \text{ rad/s}$

$\frac{R_f}{R_{in}} = 10 \rightarrow R_f = 10000, R_{in} = 1000$

2)

$$H(j\omega) = \left(\frac{-1}{1+j\omega R_L C_L} \right) \left(\frac{-R_H C_H(j\omega)}{1+j\omega R_H C_H} \right) \left(\frac{-R_f}{R_{in}} \right)$$


$$H(j\omega_{c1}) = 7.07 \angle -135.57^\circ$$

$$H(j\omega_{c2}) = 7.07 \angle 95.767^\circ$$

$$H(j\omega_0) = 9.9 \angle 180^\circ$$

$$\text{Max gain} = 10$$

(3) Simulation:

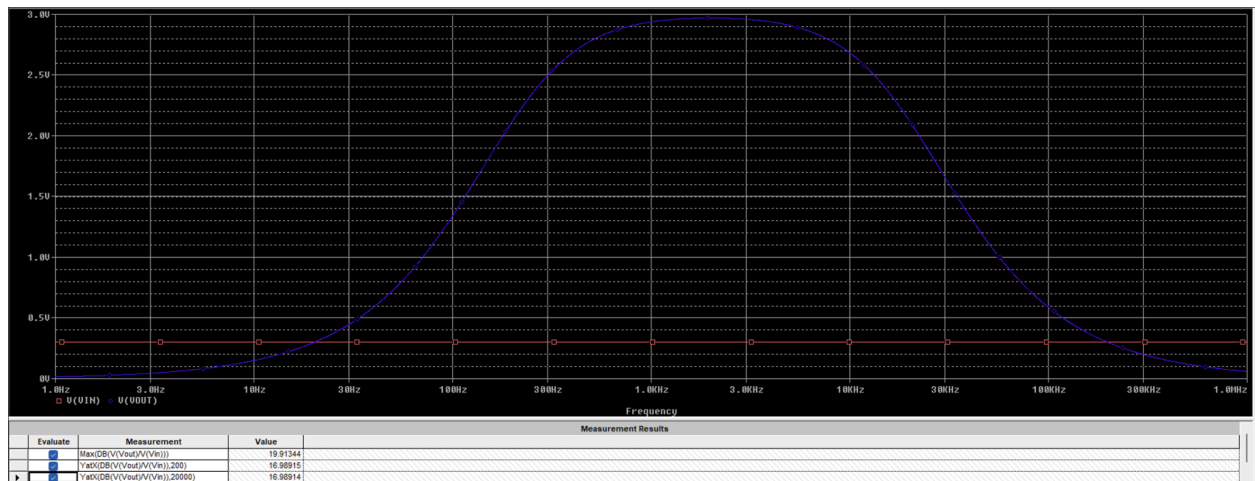

$$@ \omega_0, \text{ gain} = 19.913 \text{ dB}$$

$$20 \log(x) = 19.913 \text{ dB}$$

$$x = 9.9$$

gain of 9.9 @ ω_0 agrees with my initial calculations from part 2

$$\boxed{@ \omega_{c1}}, \text{ gain} = 16.99 \text{ dB}$$

$$20 \log(x) = 16.99$$

$$x = 7.07$$

gain of 7.07 @ ω_{c1} agrees with my initial calculations from part 2


$$\boxed{@ \omega_{c2}}, \text{ gain} = 16.99 \text{ dB}$$

$$20 \log(x) = 16.99$$


$$x = 7.07$$

gain of 7.07 @ ω_{c1} agrees with my initial calculations from part 2


(4) Experiment:

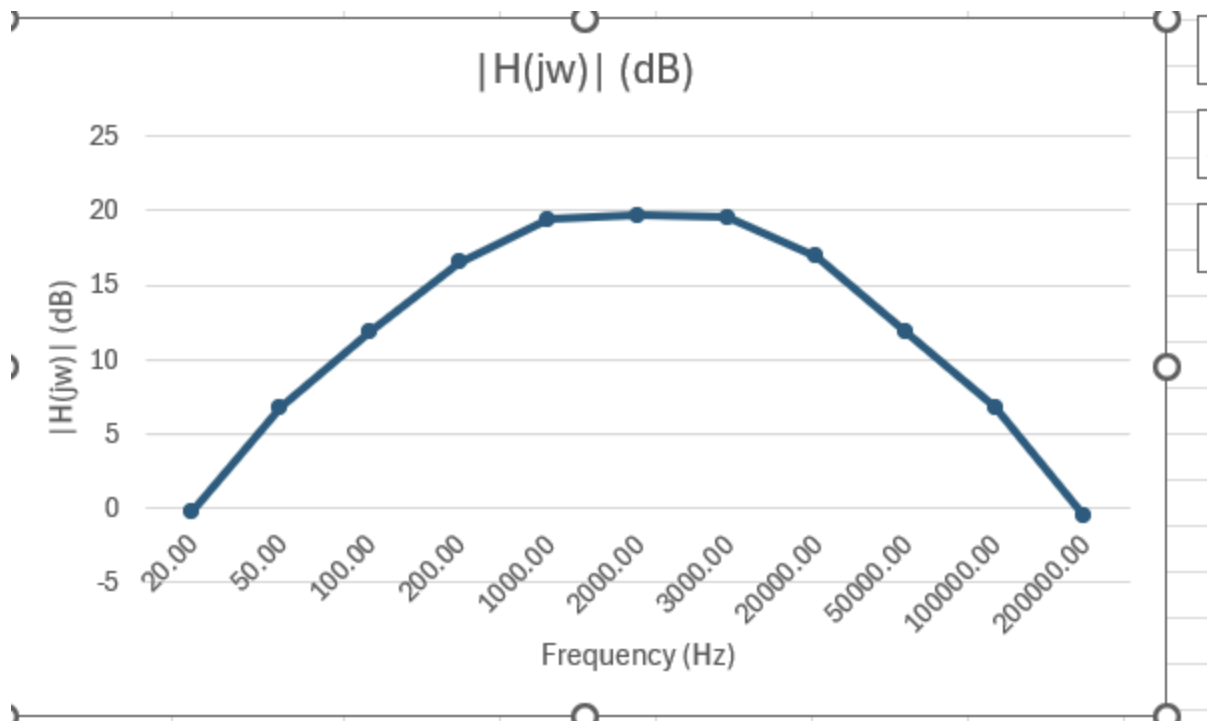



	A	B	C	D	E	F	G	H	I	J	K	L	M	N	O	P	Q	R
1	f(Hz)	Ain (Vpp)	Aout(Vpp)	H(jw)	H(jw) (dB)			f(Hz)	H(jw) (dB)									
2	20	0.64	0.62	1.03226	-0.27577			20	-0.27577									
3	50	0.64	1.4	0.45714	6.79896			50	6.79896									
4	100	0.64	2.52	0.25397	11.9044			100	11.9044									
5	200	0.64	4.3	0.14884	16.5458			200	16.5458									
6	1000	0.64	6	0.10667	19.4394			1000	19.4394									
7	2000	0.64	6.2	0.10323	19.7242			2000	19.7242									
8	3000	0.64	6.1	0.10492	19.583			3000	19.583									
9	20000	0.64	4.5	0.14222	16.9407			20000	16.9407									
10	50000	0.64	2.5	0.256	11.8352			50000	11.8352									
11	100000	0.64	1.4	0.45714	6.79896			100000	6.79896									
12	200000	0.64	0.6	1.06667	-0.56057			200000	-0.56057									
13																		
14																		
15																		
16																		
17																		
18																		
19																		
20																		
21																		
22																		
23																		
24																		

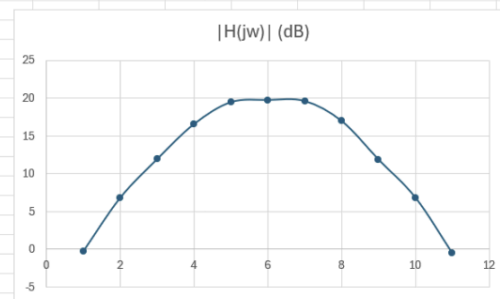



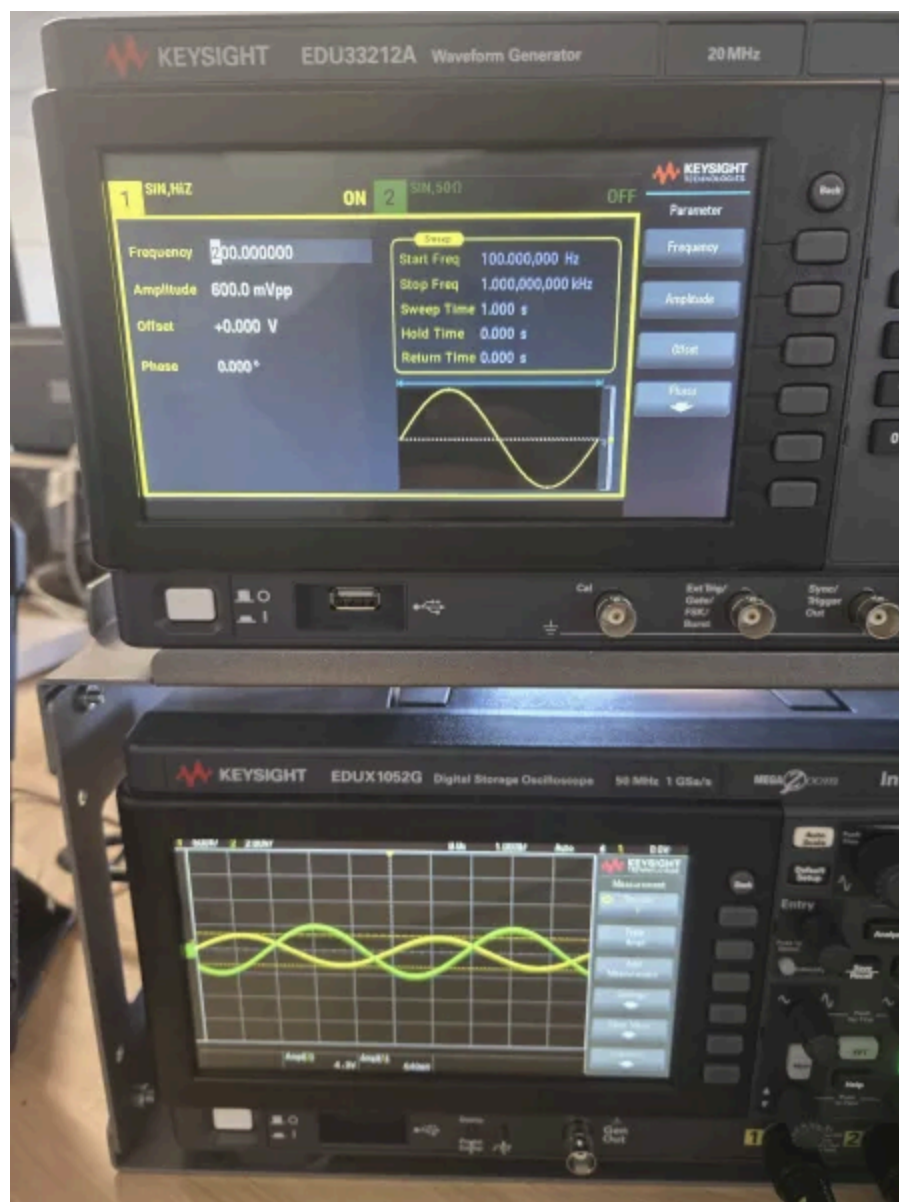

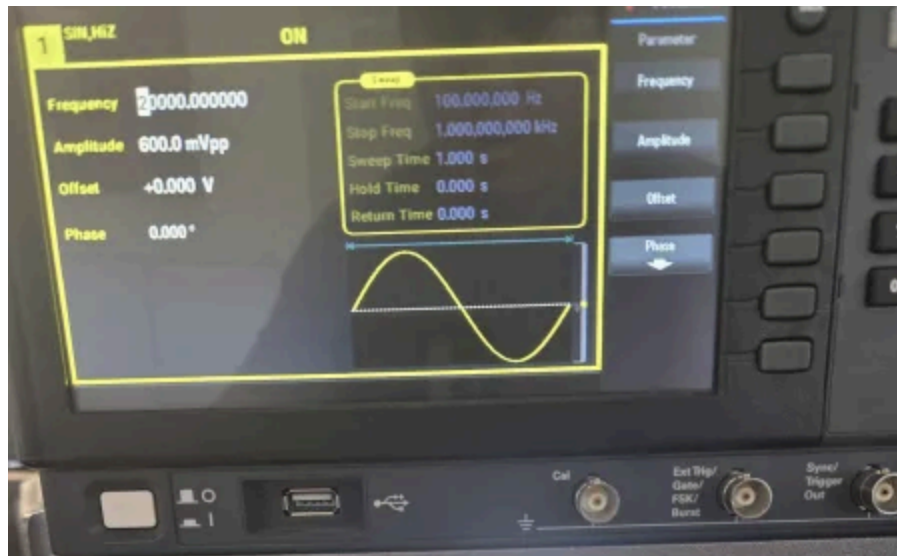

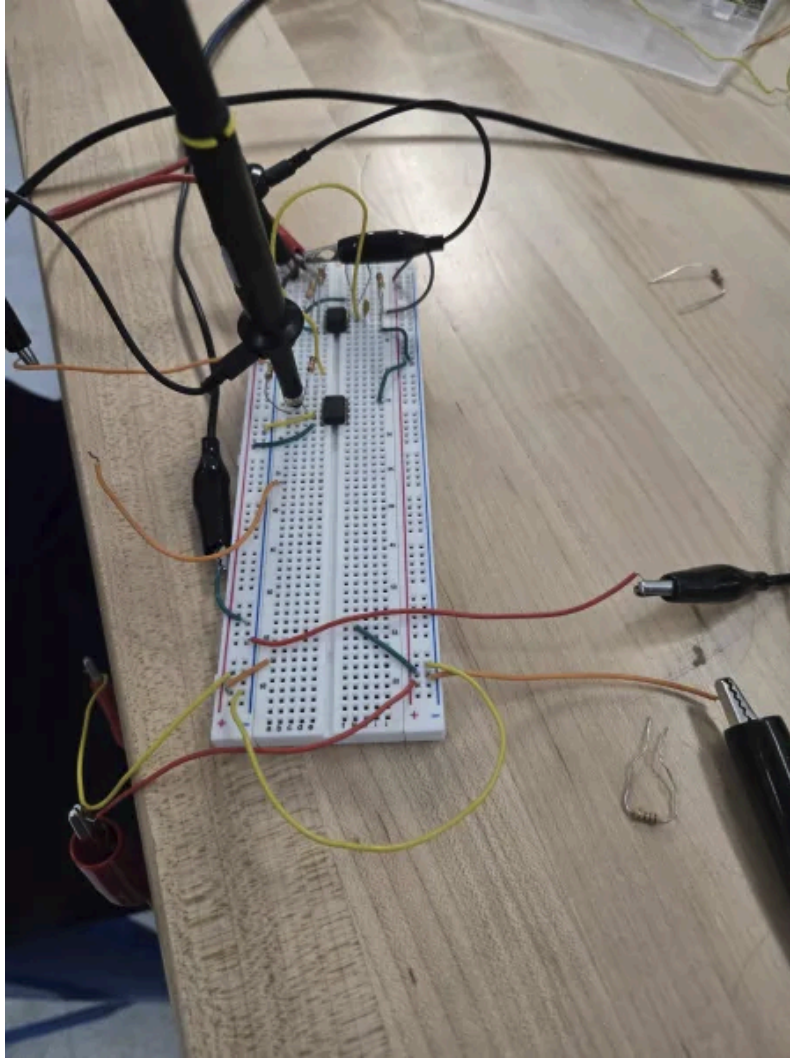

Our results meet the landline telephone specifications.

(5) Conclusion:


Our calculated values and simulated values matched the experimental values found in lab. While there is deviation due to the deviation in resistance and capacitance values, the general shape of the bode plots matched, and the cut off values were within an acceptable margin of error. By inputting a signal of various frequencies into the filter circuits, we were able to see just how the various frequencies were manipulated by the filter-whether they were let through or attenuated. Through this experiment my understanding of how active bandpass filter circuits work improved, and I can intuitively predict how a certain input signal will be affected by the filter circuit given its specifications.

(6) Checkoff:

UNIVERSITY OF CALIFORNIA, DAVIS
Department of Electrical and Computer Engineering

EEEC 100 Circuits II Fall 2024

Lab Number 6

Student Name	Pre-Lab	Simulation	Experiment	Total	T.A. Signature	Date
Daniel Navech	B	B	B			11/7/24
Justin Hsu	B	B	B			11/7/24

T.A. Comments: Send it